



# Lecture 11

## - Magnetically Coupled Circuits



# Outline



- Mutual inductance
- Transformers


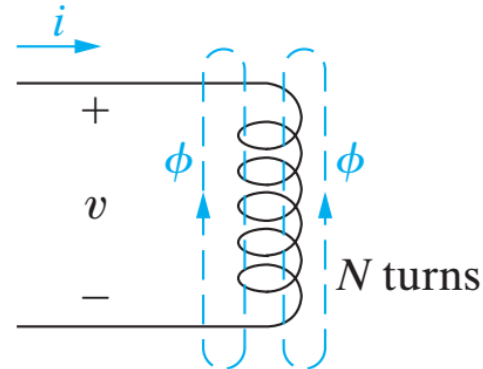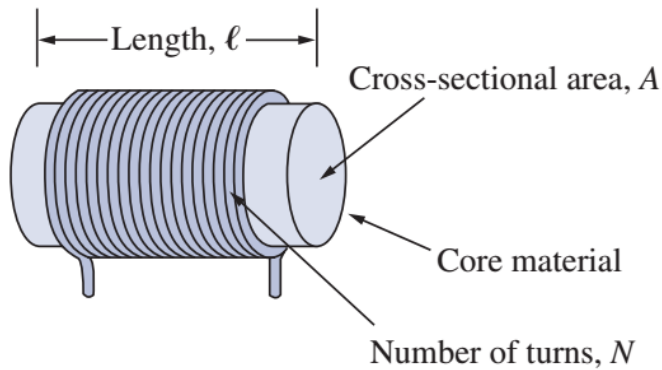
# Recall: Self Inductance

- Self inductance:

Reaction of the inductor to the change in current ***through itself***.




$$v = L \frac{di}{dt}$$


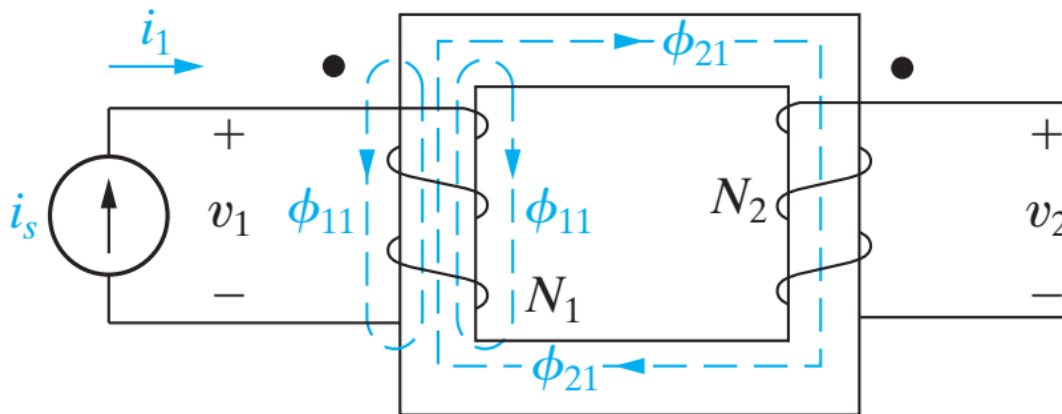
# Mutual Inductance



- Mutual inductance: Reaction of one inductor to the change in current **through another inductor.**



$$\begin{aligned} v_2 &= \frac{d(N_2\phi_{21})}{dt} = N_2 \frac{d(\mathcal{P}_{21}N_1i_1)}{dt} \\ &= N_2N_1\mathcal{P}_{21} \frac{di_1}{dt} \\ &= M_{21} \frac{di_1}{dt} \end{aligned}$$


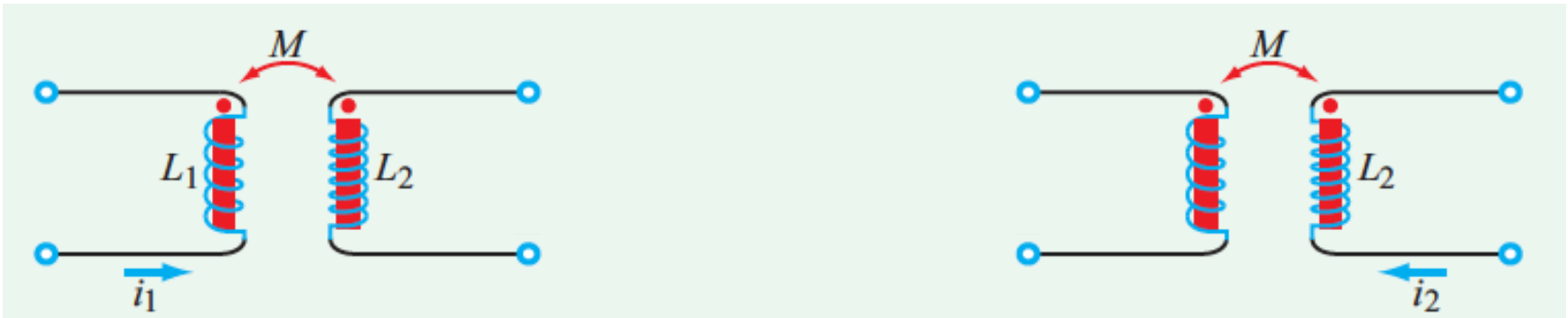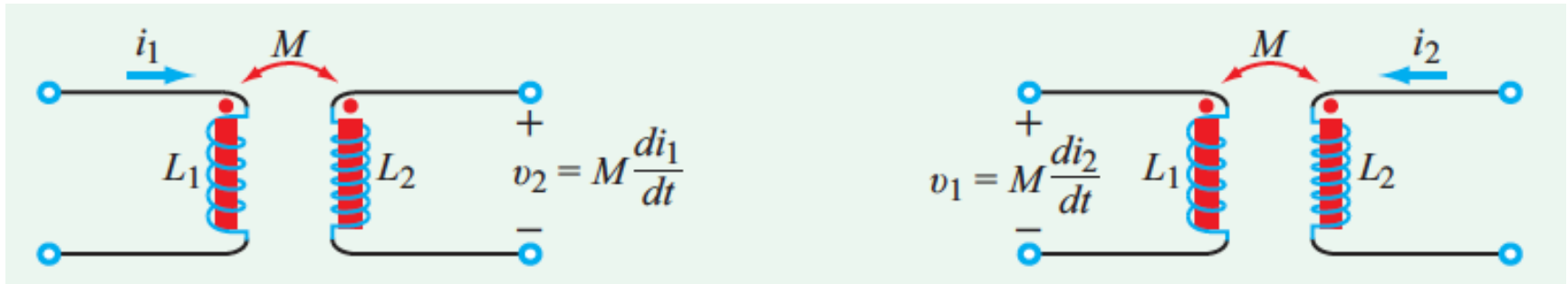
# Dot Convention: Defines Directions of Windings



If a current enters the dotted terminal of one coil, the reference polarity of mutual voltage in the 2<sup>nd</sup> coil is the positive at the dotted terminal, negative at the un-dotted terminal.





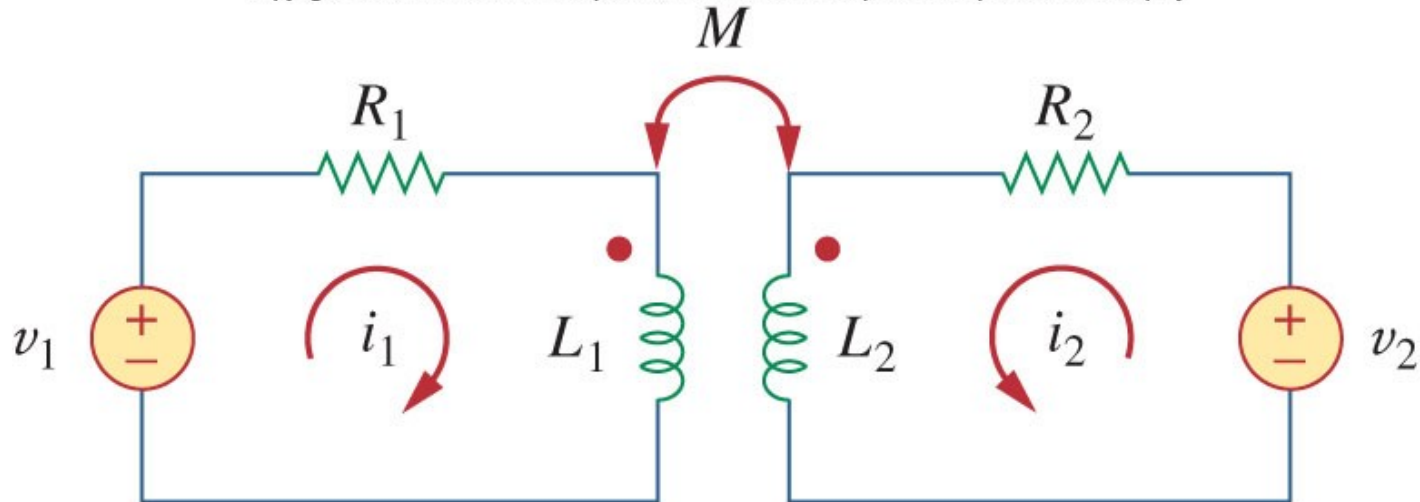
# Magnetically Coupled Circuits

- $L_1, L_2$ : self-inductances
- $M$ : mutual inductance
- Dots: indicating polarity of mutually induced voltages.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display







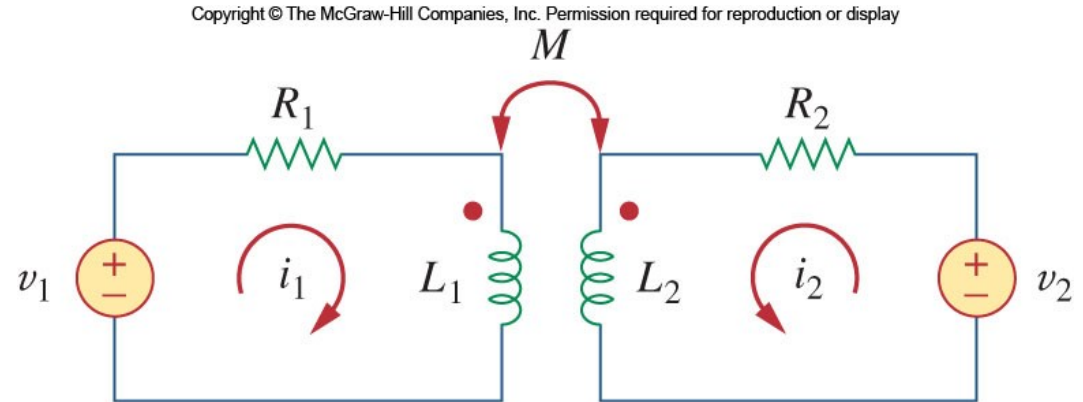
# Analysis

- Find  $i_1$  and  $i_2$ .
  - In time domain
  - In phasor domain






# Solve mutually coupled inductors

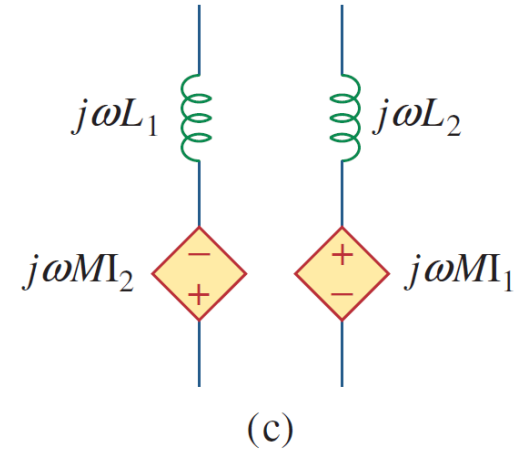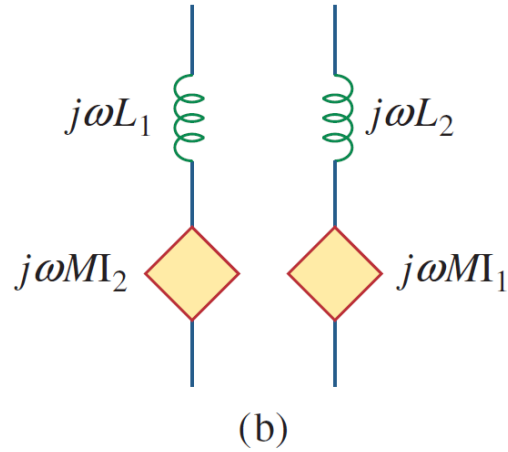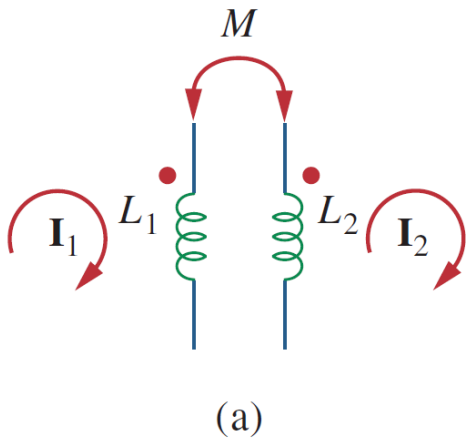


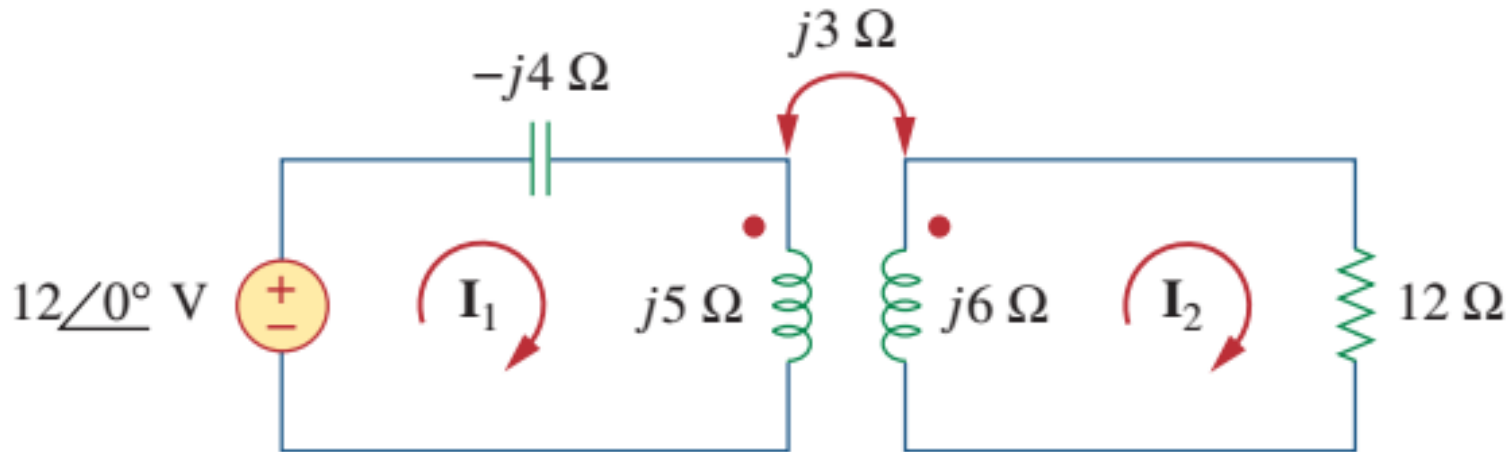
## Example

- Calculate the phasor currents  $\mathbf{I}_1$ , and  $\mathbf{I}_2$
- Calculate the phasor voltages  $\mathbf{V}_1$ , and  $\mathbf{V}_2$  across the inductors







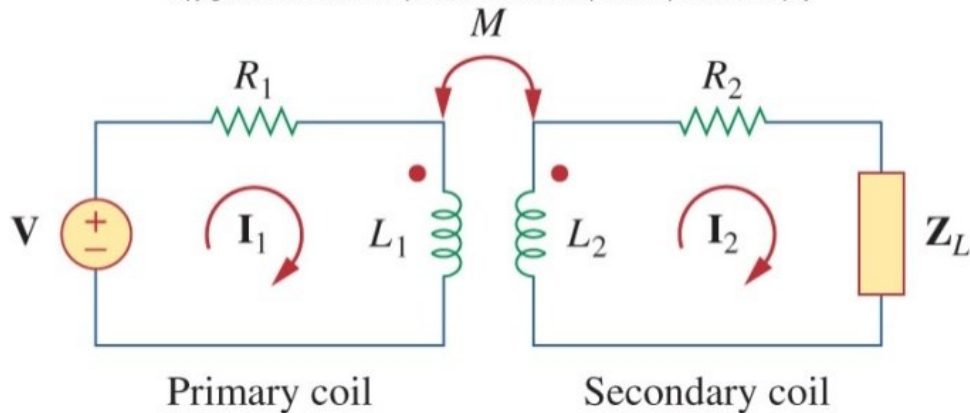
# Transformers

- A transformer is a magnetic device that takes advantage of mutual inductance.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




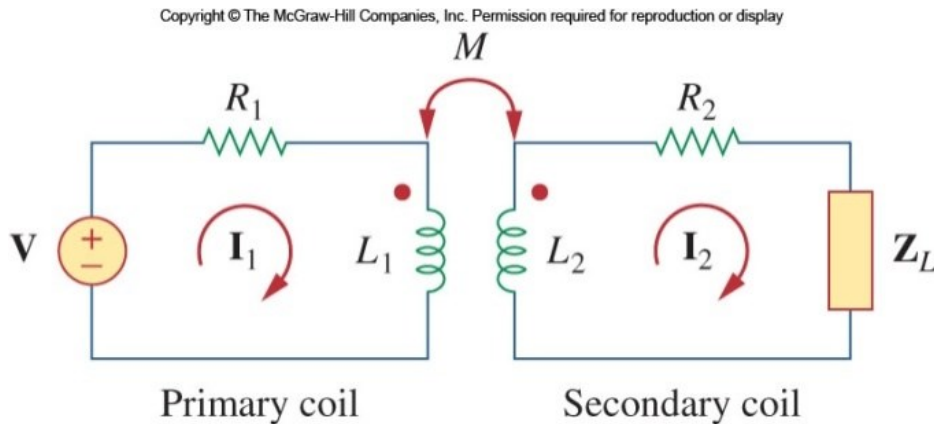
# Transformer Impedance

- An important parameter to know for a transformer is how the input impedance  $Z_{in}$  is seen from the source.




$$Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$


Reflected impedance from secondary to primary


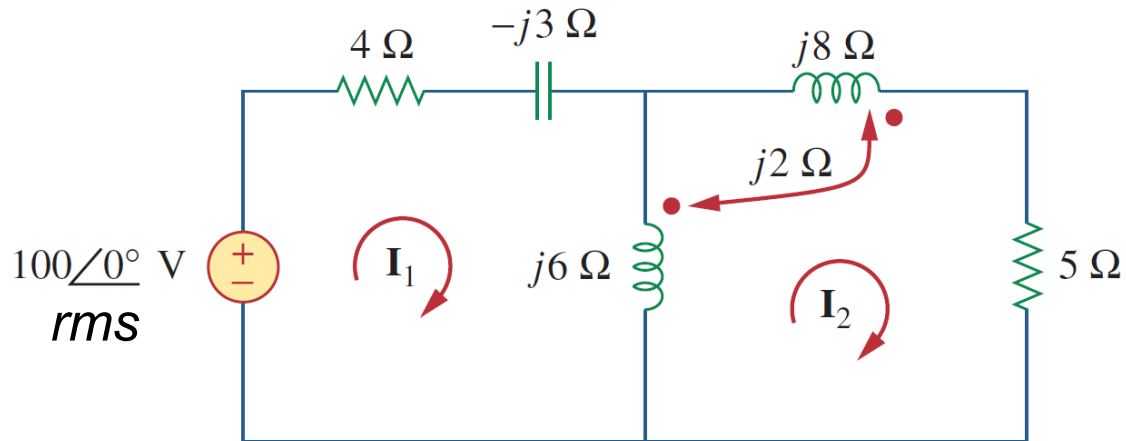
## Example

Find (1) mesh currents &  
(2) complex power absorbed by the voltage source




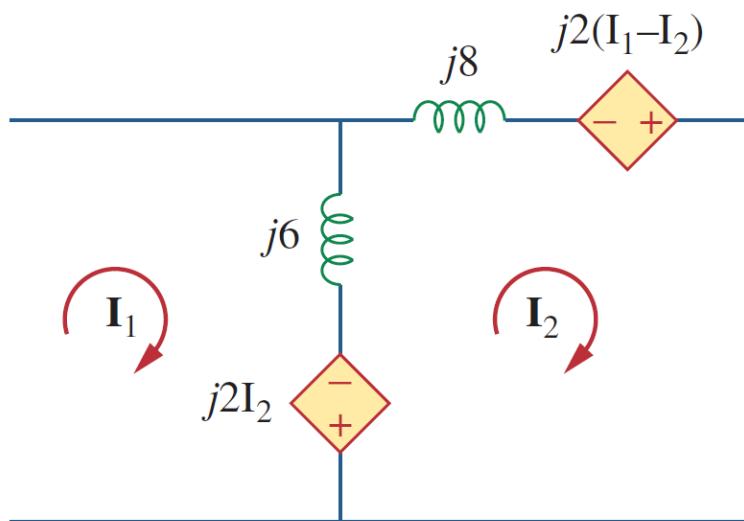


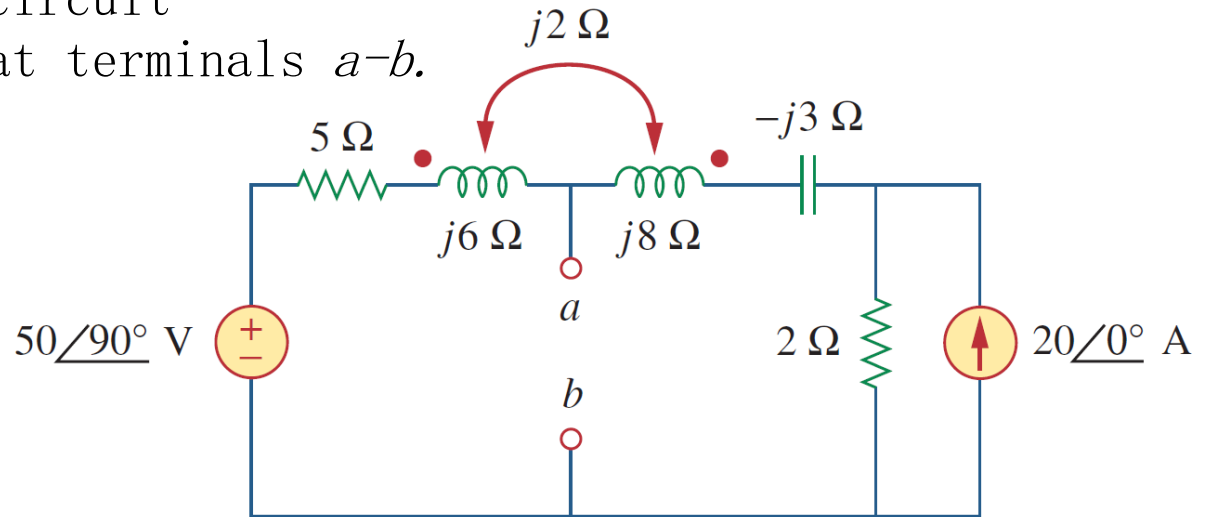
# Practice

Obtain the Thevenin equivalent circuit for the circuit at terminals  $a-b$ .




# Energy in a Coupled Circuit


- The energy stored in an inductor is
- For coupled inductors, the total energy stored is

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

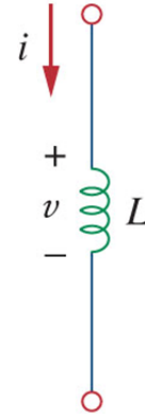- The positive sign is selected when the currents both enter or leave the dotted terminals.



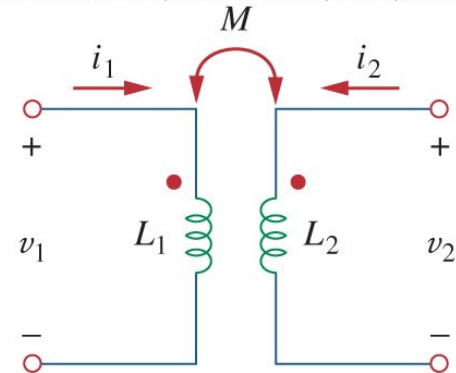Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






# Practice

If  $M = 0.2$  H

Find  $i_1$   $i_2$ .

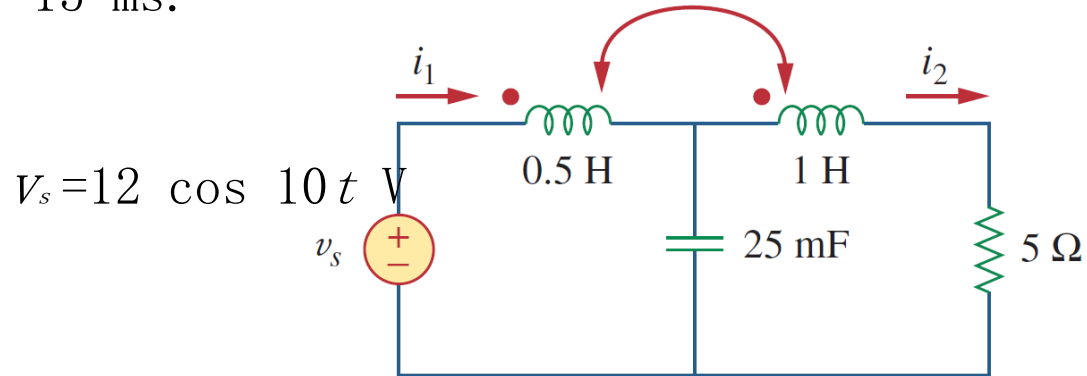Calculate the energy stored in the coupled coils at  $t = 15$  ms.





## Coupling Coefficient $k$

- The system cannot have negative energy

$$\frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 - Mi_1i_2 \geq 0 \quad \Rightarrow \quad M \leq \sqrt{L_1L_2}$$

- Define a parameter describes how closely  $M$  approaches upper limit.

$$k = \frac{M}{\sqrt{L_1L_2}}$$


- Coupling coefficient,  $0 \leq k \leq 1$ .


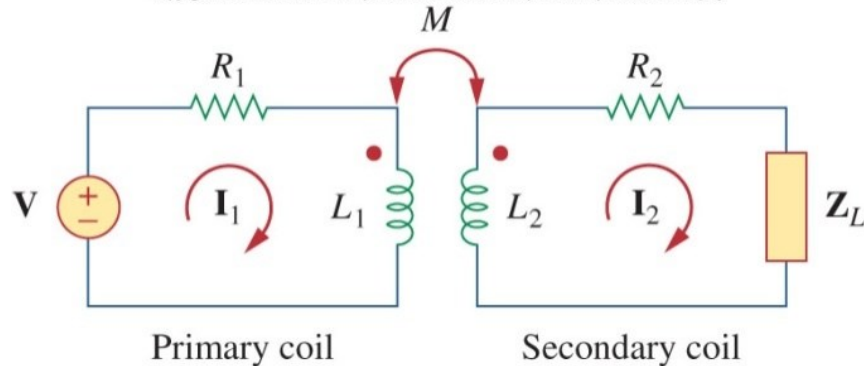
# Ideal Transformers


- The ideal transformer has:
  - Coils with very large reactance  
( $L_1, L_2, M \rightarrow \infty$ )
  - Coupling coefficient  $k=1$ .
  - Primary and secondary coils are lossless,  $R_1 = R_2 = 0$ .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





# Ideal Transformers

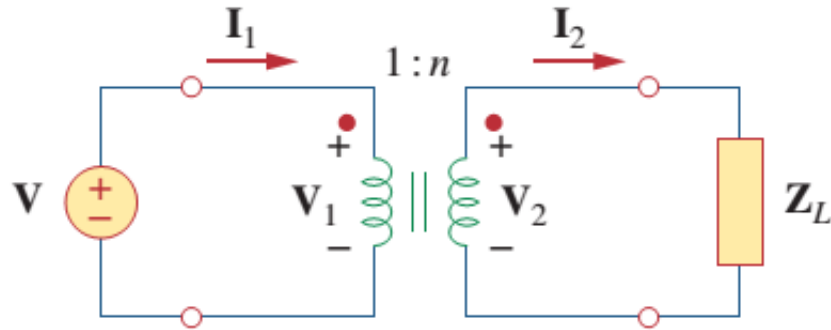

- The voltage is related as:


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n \quad (13.52)$$

- The current is related as:


$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n} \quad (13.55)$$



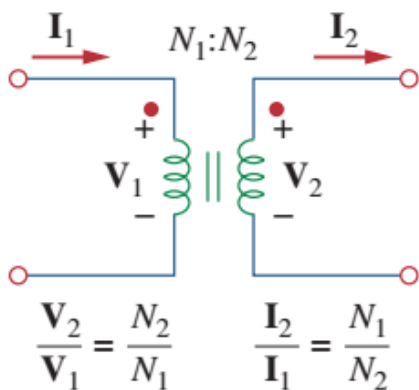
1. If  $V_1$  and  $V_2$  are *both* positive or both negative at the dotted terminals, use  $+n$  in Eq. (13.52). Otherwise, use  $-n$ .
2. If  $I_1$  and  $I_2$  *both* enter into or both leave the dotted terminals, use  $-n$  in Eq. (13.55). Otherwise, use  $+n$ .




(a)

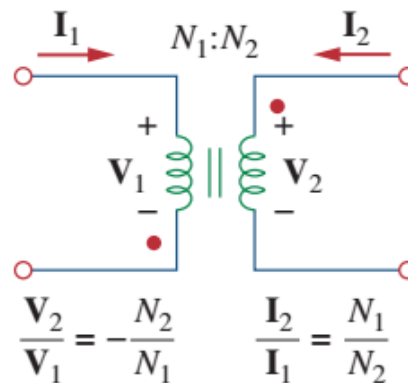

(c)

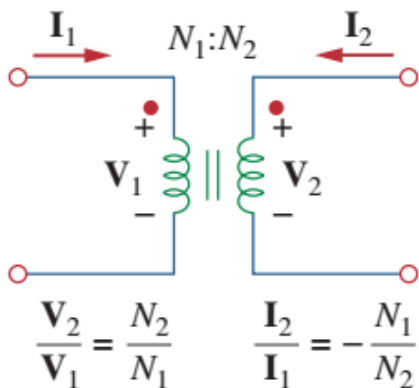


(b)

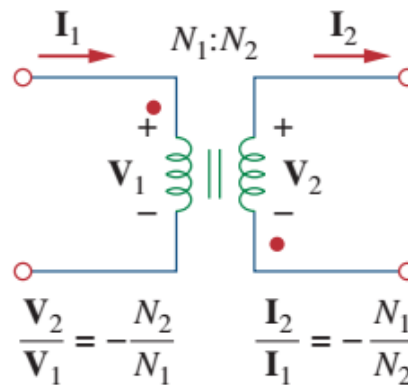


(d)




# Practice

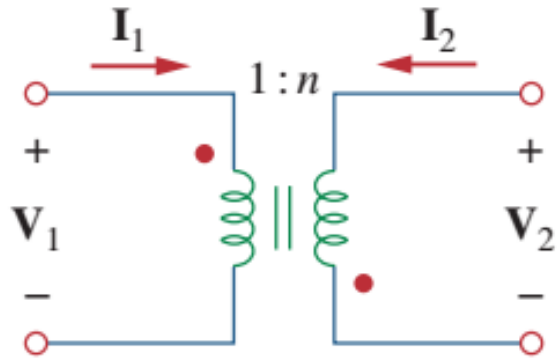


(a)

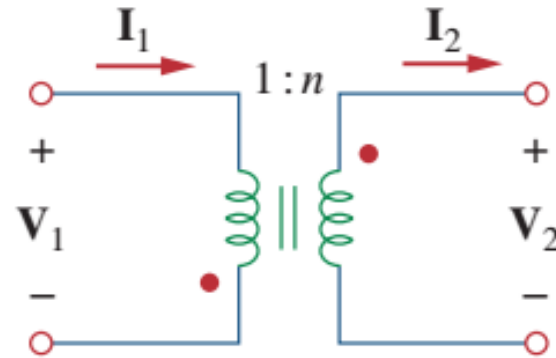

(b)

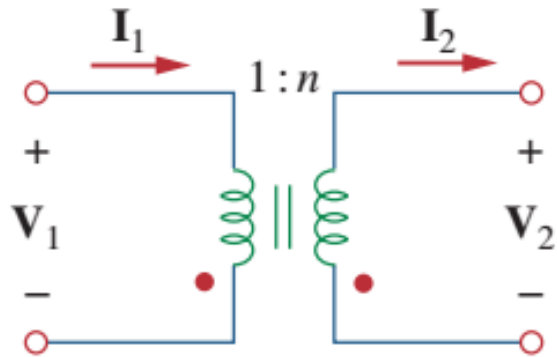

(c)

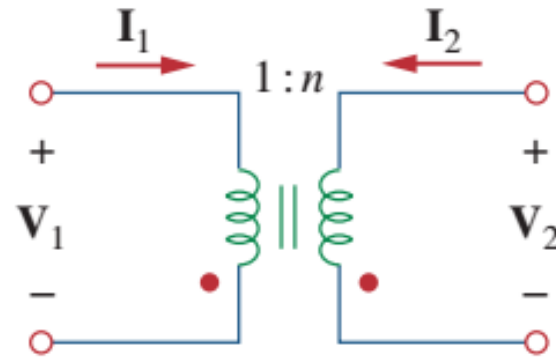


(d)





# Ideal Transformers

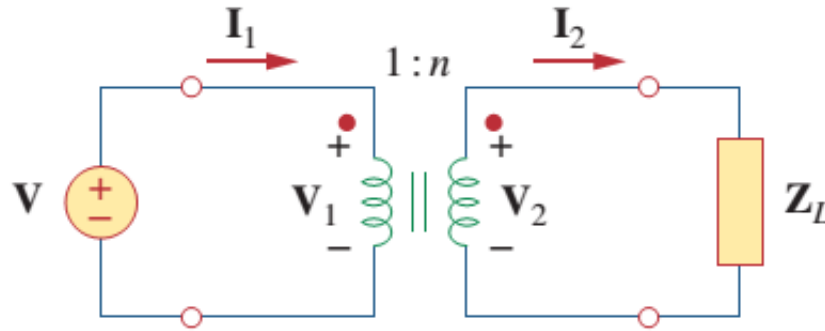


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

- Reflected impedance

$$Z_{\text{in}} = \frac{V_1}{I_1} =$$



# Ideal Transformers


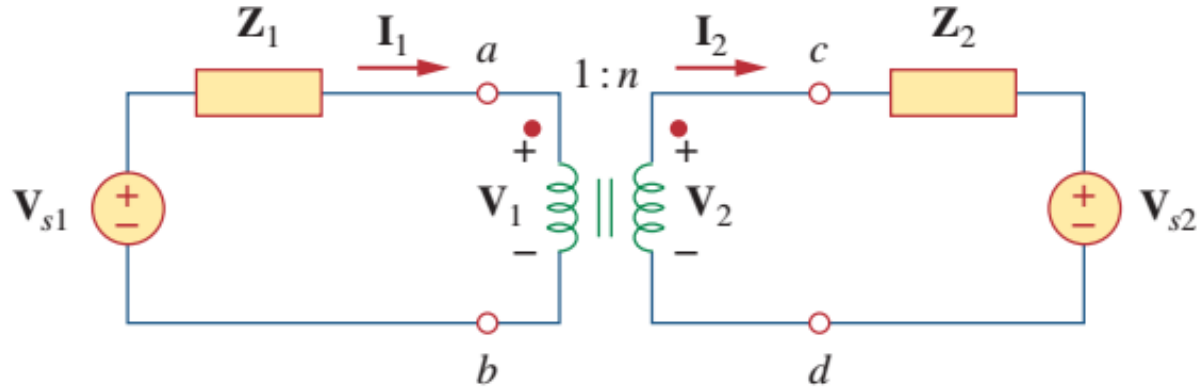



$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$





# Ideal Transformers

- Reflected impedance and source

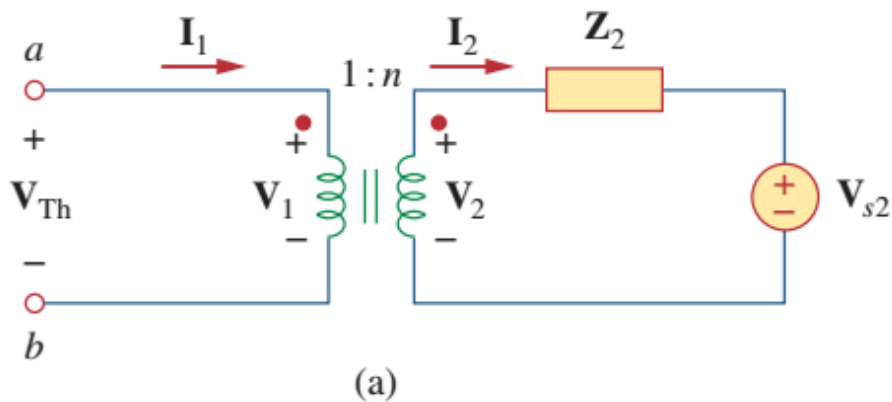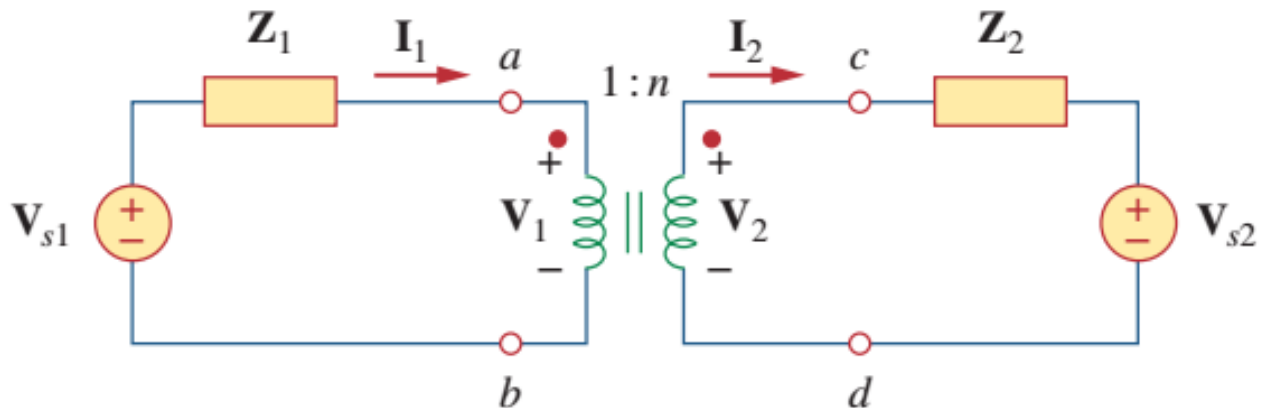

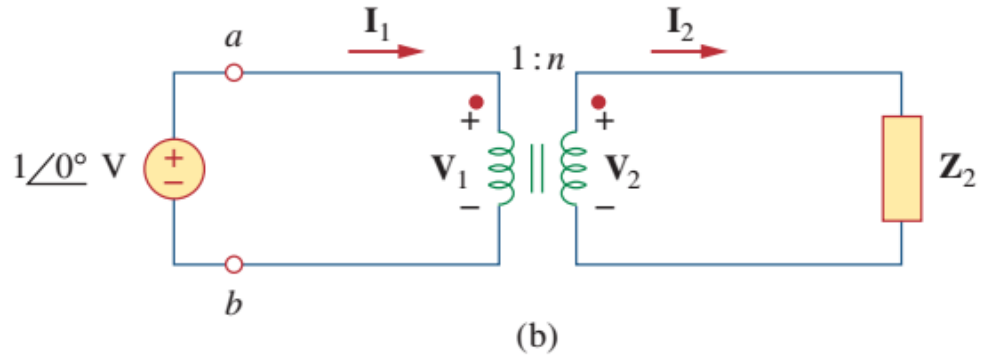


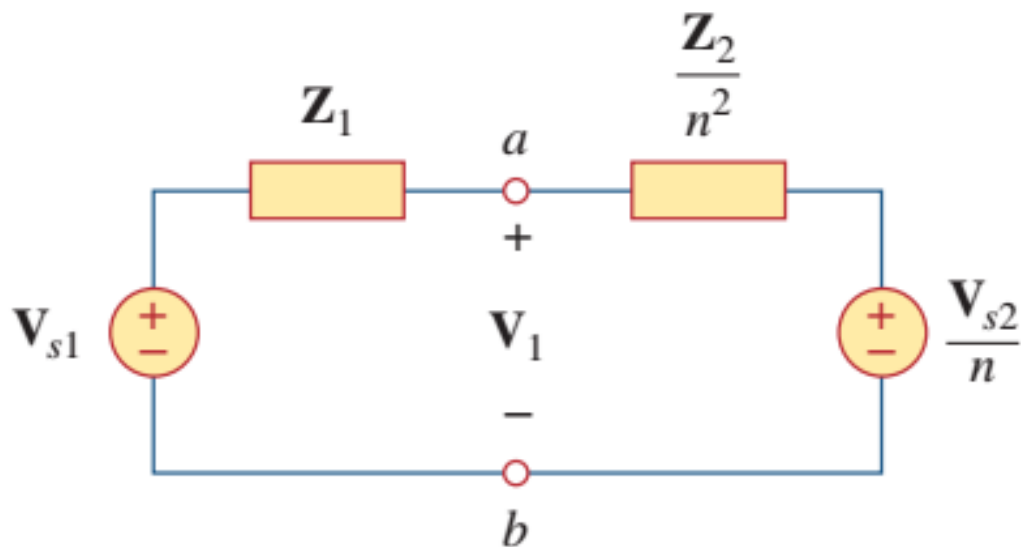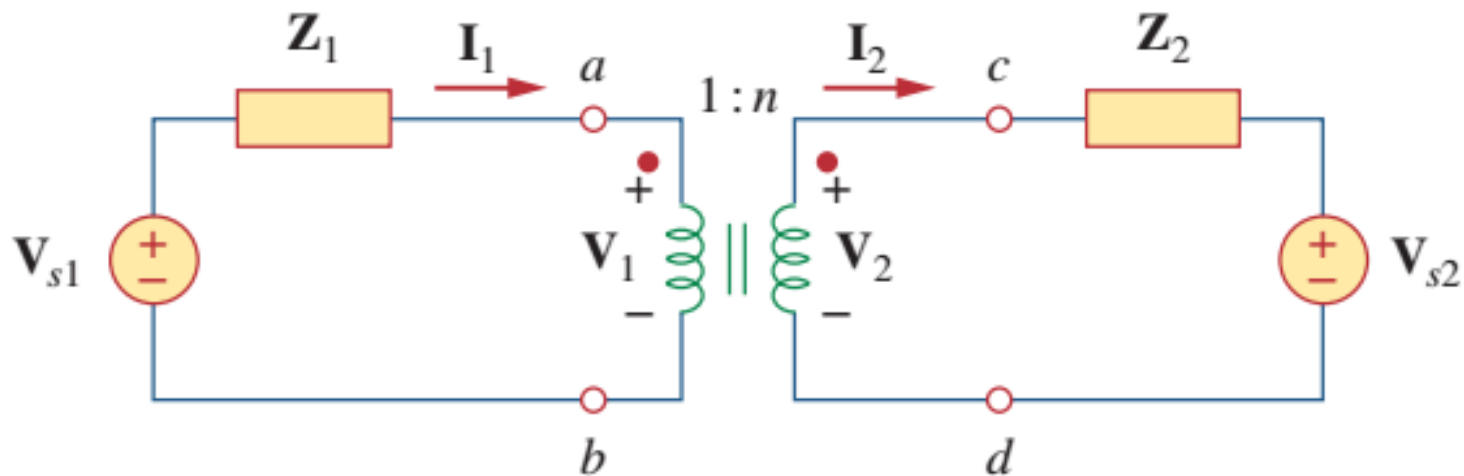



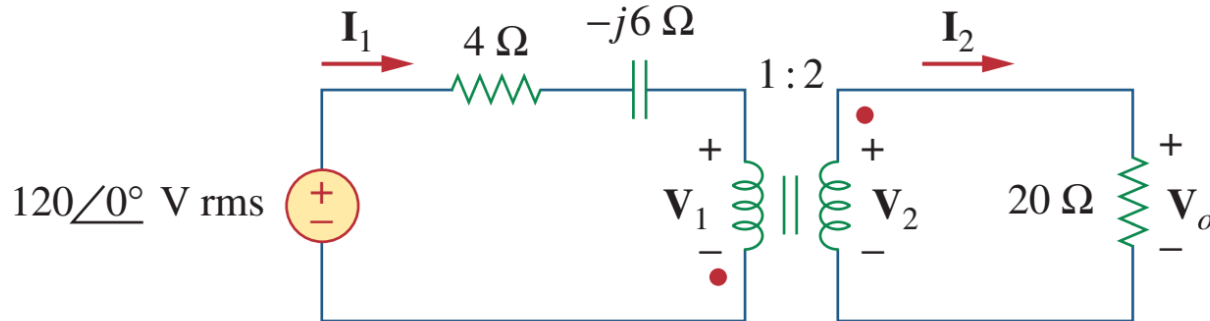
## Example

For the ideal transformer circuit of Fig. 13.37, find: (a) the source current  $\mathbf{I}_1$ , (b) the output voltage  $\mathbf{V}_o$ , and (c) the complex power supplied by the source.



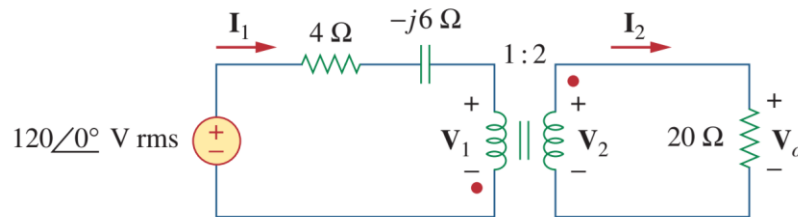

**Solution:**

(a) The 20-Ω impedance can be reflected to the primary side and we get

$$\mathbf{Z}_R = \frac{20}{n^2} = \frac{20}{4} = 5 \Omega$$

Thus,

$$\begin{aligned}\mathbf{Z}_{\text{in}} &= 4 - j6 + \mathbf{Z}_R = 9 - j6 = 10.82 \angle -33.69^\circ \Omega \\ \mathbf{I}_1 &= \frac{120 \angle 0^\circ}{\mathbf{Z}_{\text{in}}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \text{ A}\end{aligned}$$

(b) Since both  $\mathbf{I}_1$  and  $\mathbf{I}_2$  leave the dotted terminals,

$$\begin{aligned}\mathbf{I}_2 &= -\frac{1}{n} \mathbf{I}_1 = -5.545 \angle 33.69^\circ \text{ A} \\ \mathbf{V}_o &= 20 \mathbf{I}_2 = 110.9 \angle 213.69^\circ \text{ V}\end{aligned}$$


(c) The complex power supplied is

$$\mathbf{S} = \mathbf{V}_s \mathbf{I}_1^* = (120 \angle 0^\circ)(11.09 \angle -33.69^\circ) = 1,330.8 \angle -33.69^\circ \text{ VA}$$



# Practice


- Find reflected impedance and  $I_1$

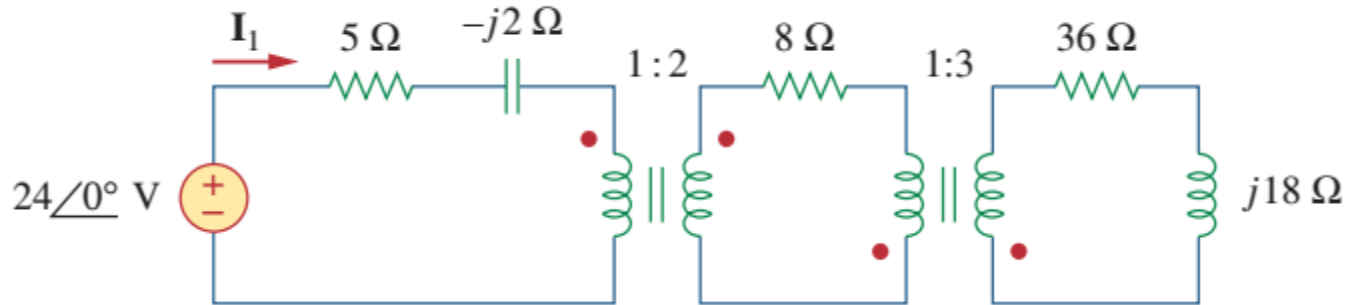


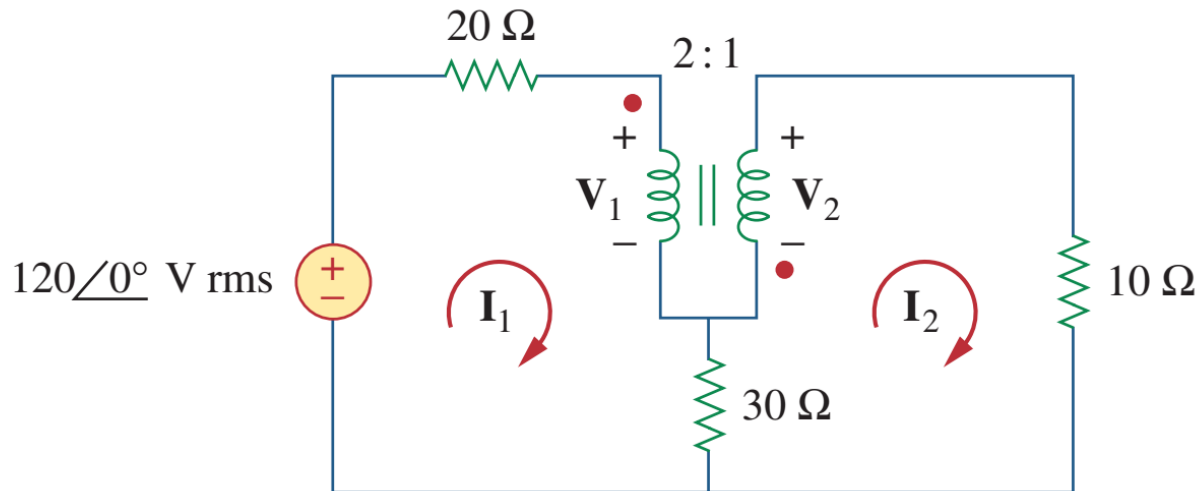
# Example

Calculate the power supplied to the  $10\text{-}\Omega$  resistor in the ideal transformer circuit of Fig. 13.39.





$$-120 + (20 + 30)\mathbf{I}_1 - 30\mathbf{I}_2 + \mathbf{V}_1 = 0$$

or

$$50\mathbf{I}_1 - 30\mathbf{I}_2 + \mathbf{V}_1 = 120 \quad (13.9.1)$$

For mesh 2,

$$-\mathbf{V}_2 + (10 + 30)\mathbf{I}_2 - 30\mathbf{I}_1 = 0$$

or

$$-30\mathbf{I}_1 + 40\mathbf{I}_2 - \mathbf{V}_2 = 0 \quad (13.9.2)$$

At the transformer terminals,

$$\mathbf{V}_2 = -\frac{1}{2}\mathbf{V}_1 \quad (13.9.3)$$

$$\mathbf{I}_2 = -2\mathbf{I}_1 \quad (13.9.4)$$

(Note that  $n = 1/2$ .) We now have four equations and four unknowns, but our goal is to get  $\mathbf{I}_2$ . So we substitute for  $\mathbf{V}_1$  and  $\mathbf{I}_1$  in terms of  $\mathbf{V}_2$  and  $\mathbf{I}_2$  in Eqs. (13.9.1) and (13.9.2). Equation (13.9.1) becomes

$$-55\mathbf{I}_2 - 2\mathbf{V}_2 = 120 \quad (13.9.5)$$

and Eq. (13.9.2) becomes

$$15\mathbf{I}_2 + 40\mathbf{I}_2 - \mathbf{V}_2 = 0 \quad \Rightarrow \quad \mathbf{V}_2 = 55\mathbf{I}_2 \quad (13.9.6)$$

Substituting Eq. (13.9.6) in Eq. (13.9.5),

$$-165\mathbf{I}_2 = 120 \quad \Rightarrow \quad \mathbf{I}_2 = -\frac{120}{165} = -0.7272 \text{ A}$$

The power absorbed by the  $10\text{-}\Omega$  resistor is

$$P = (-0.7272)^2(10) = 5.3 \text{ W}$$